INDEX

S. No.	Topic Name	Page No.	Remark	Sign
1	1×4 Demultiplexer	1		
2	2×4 Decoder	1		
3	3×8 Decoder	2		
4	4×1 Multiplexer	3		
5	8×1 Multiplexer	3		
6	Octal to Binary encoder	5		
7	Decimal to BCD encoder	6		
8	2×1 Multiplexer	7		
9	3 bit even parity generator using NAND gate	7		
10	4 bit even parity generator using NAND gate	8		
11	And gate using NAND gate	8		
12	And gate using NOR gate	8		
13	D flip flop using NAND gate	9		
14	Excess 3 code conversion from BCD	9		
15	Full adder	10		
16	Full subtractor	10		
17	Half adder	11		
18	Half subtractor	11		
19	Implementation of three variable Boolean expression using basic Gates	11		
20	Implementation of three variable Boolean expression using NAND gates	12		
21	JK FLIP FLOP using NAND GATE	12		
22	Hexadecimal to binary encoder	13		
23	NAND gate using NOR gate	14		
24	NOR gate using NAND gate	14		
25	OR gate using NAND gate	15		
26	OR gate using NOR gate	15		
27	SR flip flop using NAND gate	15		
28	SR flip flop using NOR gate	16		
29	SR latch using NAND gate	16		
30	SR latch using NOR gate	16		
31	Seven segment display 3 bit	17		
32	XNOR gate using NAND gate	18		
33	XNOR gate using NOR gate	18		

S. No.	Topic Name	Page No.	Remark	Sign
34	XOR gate using NAND gate	18		
35	XOR gate using NOR gate	18		
36	AND gate	19		
37	OR Gate	19		
38	NOT gate	19		
39	XOR gate	19		
40	XNOR gate	19		
41	NOR gate	20		
42	NAND gate	20		
43	T flip flop	20		
44	Implementation of three variable Boolean expression using NOR gates	20		
45	Implementation of four variable Boolean expression using basic Gates	21		
46	Implementation of four variable Boolean expression using NAND gate	22		
47	NOT gate using NAND gate	22		
48	NOT gate using NOR gate	22		
49	Implementation of two variable Boolean expression using basic Gates	23		
50	Implementation of two variable Boolean expression using NAND gate	23		